

How to connect a TLK 33 to an DC H bridge in order to drive peltier with a current higher than 6 A

